

Binary Logics:

→ Consist of binary variables and logical operation

- A, B, C, x, y, z
- possible values $[0, 1]$
- AND
- OR
- NOT
- etc.

Logic Gates:

- Most Basic Digital Device
- 1 or more input & 1 outputs
- Output follows a certain logics

Truthtable:

→ A list of all possible inputs and outputs

All logic gates


NOT, AND, OR, XOR
NAND, NOR, XNOR

* NOT, AND, OR are Basic gates.

* NAND & NOR are universal gate.

A universal gate is a gate which can implement any other gate.


AND:

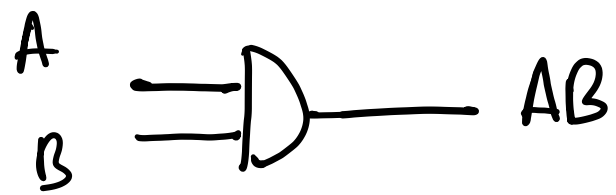

* Output 1 when all inputs are 1.

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1


OR:

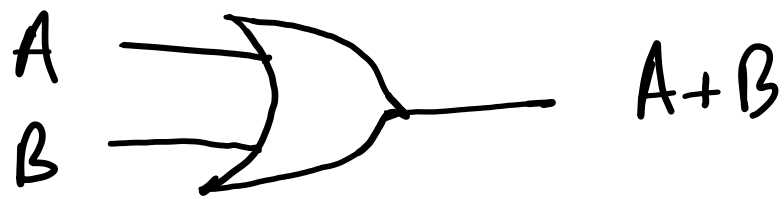

* Output 1 when atleast one input is 1

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1


NOT (Inverter)

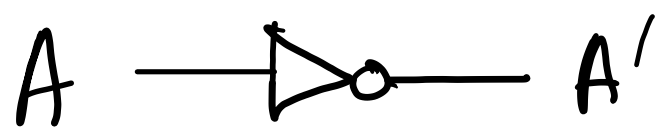


A	A'
0	1
1	0

* Output is inverse of input

NAND

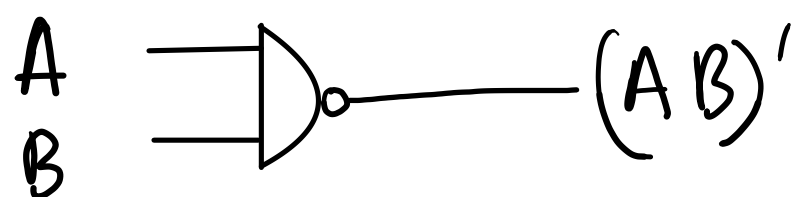


aka

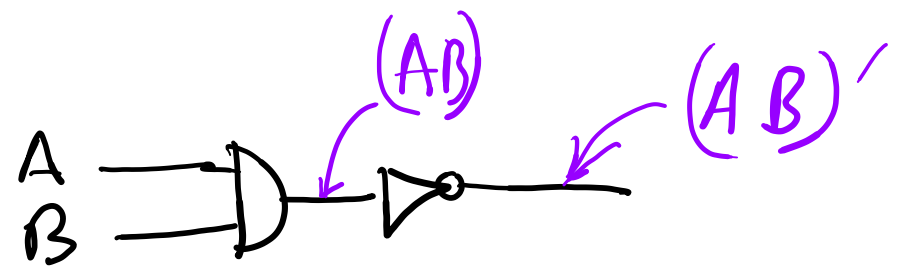


A	B	(AB)'
0	0	1
0	1	1
1	0	1
1	1	0

* Inverse of AND

NOR

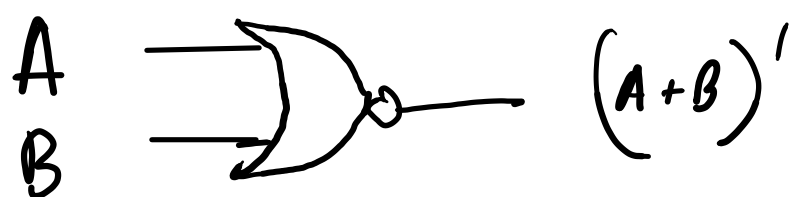


aka

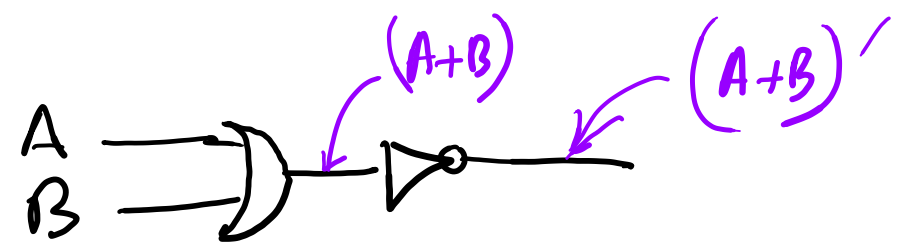

A	B	(A+B)'
0	0	1
0	1	0
1	0	0
1	1	0

* Inverse of OR


XOR

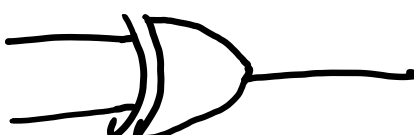A
 B  $A \oplus B = AB' + A'B$

Output 1 if odd number of input is 1

A	B	$(A \oplus B)'$
0	0	0
0	1	1
1	0	1
1	1	0


XNOR :

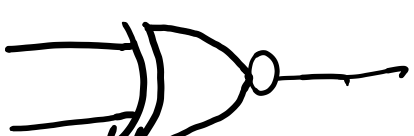A
 B  $A \odot B = AB + A'B$

A	B	$(A \odot B)'$
0	0	1
0	1	0
1	0	0
1	1	1


Inverse of XOR

Basic Gates using NAND :


NAND A
 B  $(AB)'$


NOT

A  A'

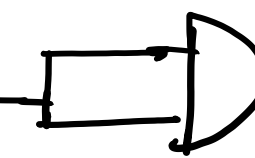
A  $(AA)' = A'$


AND

A
 B  AB

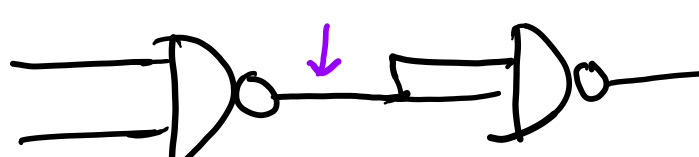A
 B  $((AB)')' = AB$

OR

A
 B  $A+B$

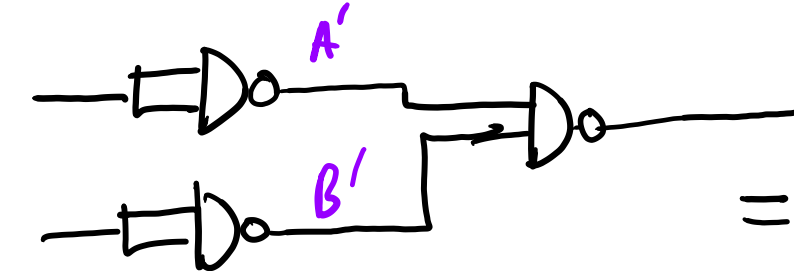A  $(A'B')'$
 B $= (A')' + (B')'$
 $= A+B$

→ Using DeMorgan's law

Basic Gates using NOR :

NOR $A \quad B \Rightarrow \neg(A+B)$

NOT $A \Rightarrow A'$

OR $A \quad B \Rightarrow A+B$

AND $A \quad B \Rightarrow AB$

$A \Rightarrow (A+A)' = A'$

$A \quad B \Rightarrow ((A+B)')' = A+B$

$A \quad B \Rightarrow (A'+B')' = (A')' \cdot (B')' = AB$
 Demorgan's law

Proof using Truth table:


* Proof that $\underbrace{x \cdot (y+z)}_{LHS} = \underbrace{(x \cdot y) + (x \cdot z)}_{RHS}$

<u>x</u>	<u>y</u>	<u>z</u>	<u>y+z</u>	<u>$x \cdot (y+z)$</u>	<u>$x \cdot y$</u>	<u>$x \cdot z$</u>	<u>$(x \cdot y) + (x \cdot z)$</u>
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

$\therefore LHS = RHS$

Implement $(AB)c' + (A' + B' + cA')$ using Basic Gates

A B C

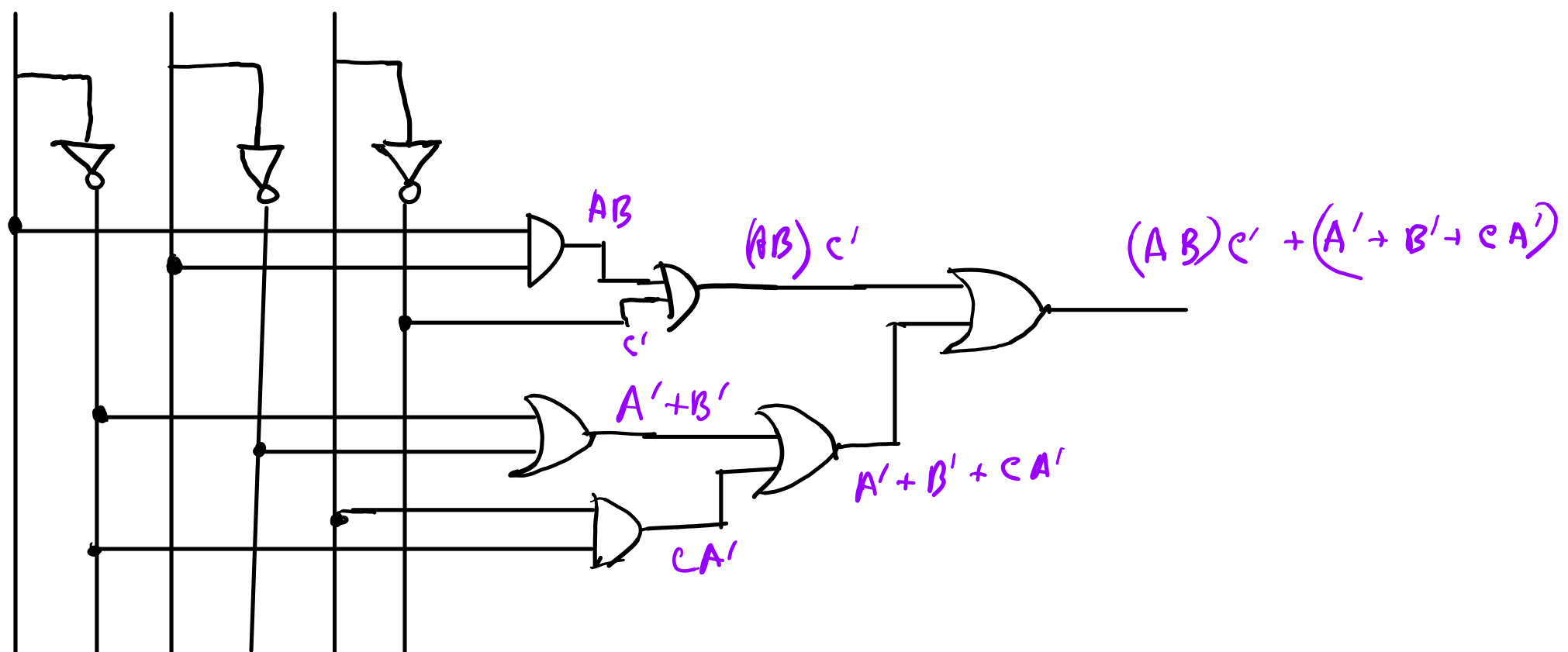

Boolean Algebra

Basic theorem of Boolean Algebra

* Theorem can be proved using Truth table or Algebraic Manipulation

Basic Theorems are:

$\Rightarrow x + 0 = x$	$x \cdot 1 = x$	Identity
$\Rightarrow x + x' = 1$	$x \cdot x' = 0$	
$\Rightarrow x + x = x$	$x \cdot x = x$	complement
$\Rightarrow x + 1 = 1$	$x \cdot 0 = 0$	
$\Rightarrow (x')' = x$		
$\Rightarrow x + y = y + x$	$x \cdot y = y \cdot x$	
$\Rightarrow x(yz) = (xy)z$	$x + (y + z) = (x + y) + z$	commutative
* $\Rightarrow x(y + z) = xy + xz$	* $x + yz = (x + y)(x + z)$	
* $\Rightarrow (x + y)' = x'y'$	* $(xy)' = x' + y'$	Distributive
* $\Rightarrow x + xy = x$	* $x(x + y) = x$	
		De Morgan
		Absorption

* All are important but student tend to forget star marked ones while simplifying

Duality Principle :

* If we interchange operators and elements as follows,

$$(OR) + \rightleftharpoons \cdot (AND)$$

$$0 \rightleftharpoons 1$$

Example:

$$\text{if } \underline{a} + (\underline{b} \cdot \underline{c}) + \underline{0} = (\underline{a} + \underline{b}) \cdot (\underline{a} + \underline{c}) \cdot \underline{1}$$

then we can find its dual expression

$$\underline{a} \cdot (\underline{b} + \underline{c}) \cdot \underline{1} = (\underline{a} \cdot \underline{b}) + (\underline{b} \cdot \underline{c}) + \underline{0}$$

* Duality Gives us free theorems

If a theorem/expression for example,

$$x + 1 = 1 \quad \text{is valid / Proved.}$$

then its dual expression,

$$x \cdot 0 = 0 \quad \text{is also valid / proved}$$

Operator Precedence:

Parentesis \longrightarrow NOT \longrightarrow AND \longrightarrow OR
Highest Lowest

Boolean Expression simplification: (Using Boolean Algebraic Manipulation)

* Simplify: $(\underline{x'y'z}) + (\underline{x'yz}) + (\underline{xy'})$

$$= \underline{x'z} (\underline{y+y'}) + xy'$$

$$= x'z \cdot 1 + xy'$$

$$= x'z + xy'$$

* Simplify:

$$\underline{xy} + \underline{xy'}$$

$$= x(\underline{y+y'}) = x \cdot 1 = x$$

* Simplify:

$$\underline{BC} + AB' + AB + \underline{BCD}$$

$$= \underline{BC} (\underline{1+D}) + AB' + AB$$

$$= BC \cdot 1 + \underline{AB'} + \underline{AB}$$

$$= BC + A(\underline{B'+B})$$

$$= BC + A \cdot 1$$

$$= BC + A$$

Prove, $(A \oplus B)' = A \odot B$ using

Boolean Manipulation:

$$\begin{aligned}
 & (A \oplus B)' \\
 = & (AB' + A'B)' \\
 = & (AB')' \cdot (A'B)' \quad \rightarrow \text{Applied DeMorgan} \\
 = & (A' + B'') \cdot (A'' + B') \quad \rightarrow \text{" " " "} \\
 = & (A' + B) \cdot (A + B') \quad \rightarrow \\
 = & \underbrace{AA'}_0 + A'B' + BA + \underbrace{BB'}_0 \\
 = & A'B' + BA \\
 = & AB + A'B' \\
 = & A \odot B
 \end{aligned}$$

Practice more & more.

Complement of a function:

if $F = (x+y)$, then its complement is $F' = (x+y)'$

However, we can also find complement of a function by

1. Taking Dual of the function
2. Complement each variables

Example:

$$F = x'y'z' + x'y'z$$

$$1. \text{ Dual} = (x' + y + z') \cdot (x' + y' + z)$$

2. Complement each var = $(x + y' + z) \cdot (x + y + z')$ = F

* Find complement of $x(y'z' + yz)$

$$1. \text{ Dual} = x + ((y' + z') \cdot (y + z))$$

$$2. \text{ Complement} = x' + (y + z) \cdot (y' + z')$$


$$\therefore F' = x' + (y + z)(y' + z')$$

Using NAND or NOR to Draw circuit of a function:

Steps:

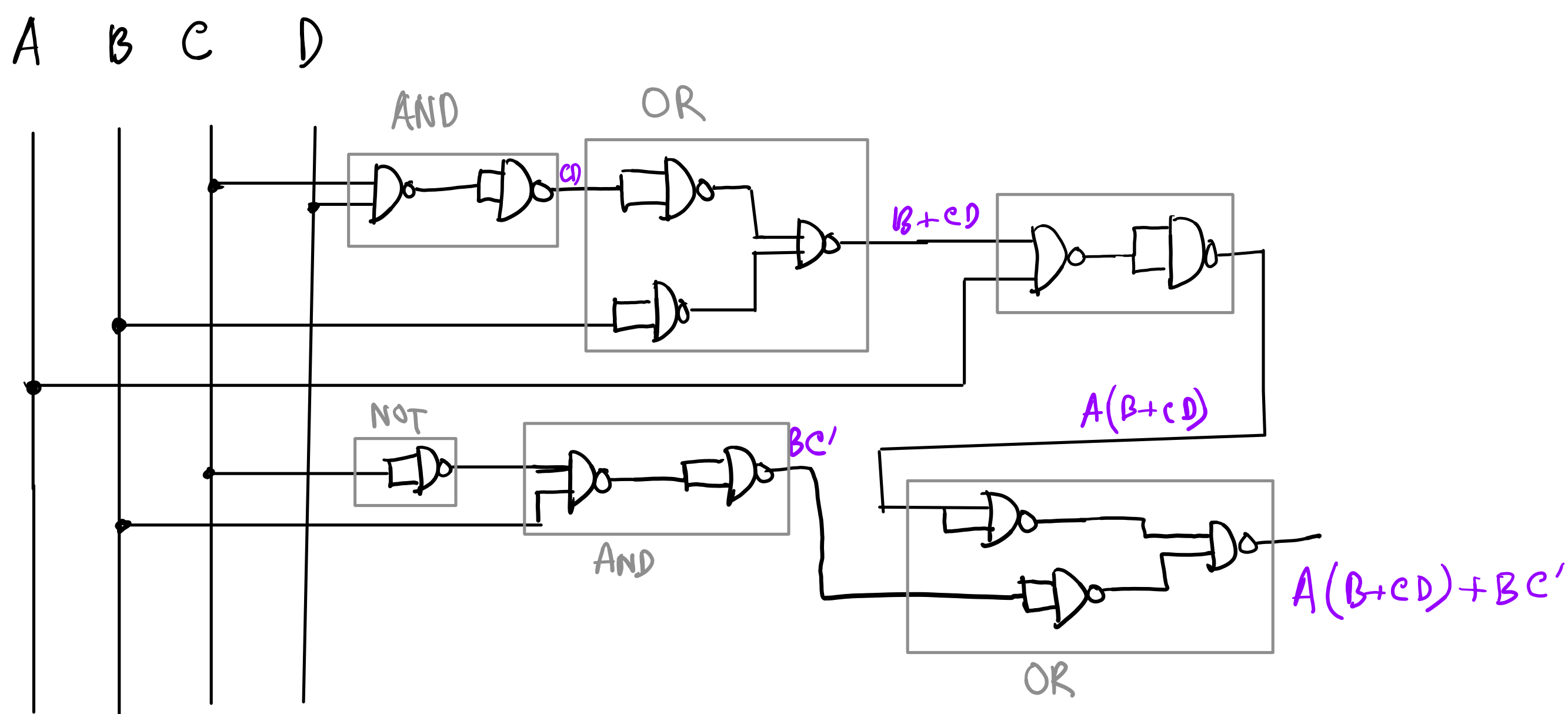1. Represent the expression using AND, OR, NOT gate.
2. Draw each gate with equivalent NAND/NOR representation.
3. Remove any 2 cascading inverter.
4. Remove inverter from single input connection and replace input with its complement. (Only if there is a constraint)


Implement $F = A(B + CD) + BC'$ using NAND only.



Now, if we want to reduce number of gates, we can remove cascading inverters.

$$\cancel{x} \text{ --- } \cancel{x'} \text{ --- } \cancel{x} = x \text{ ---}$$

A B C D

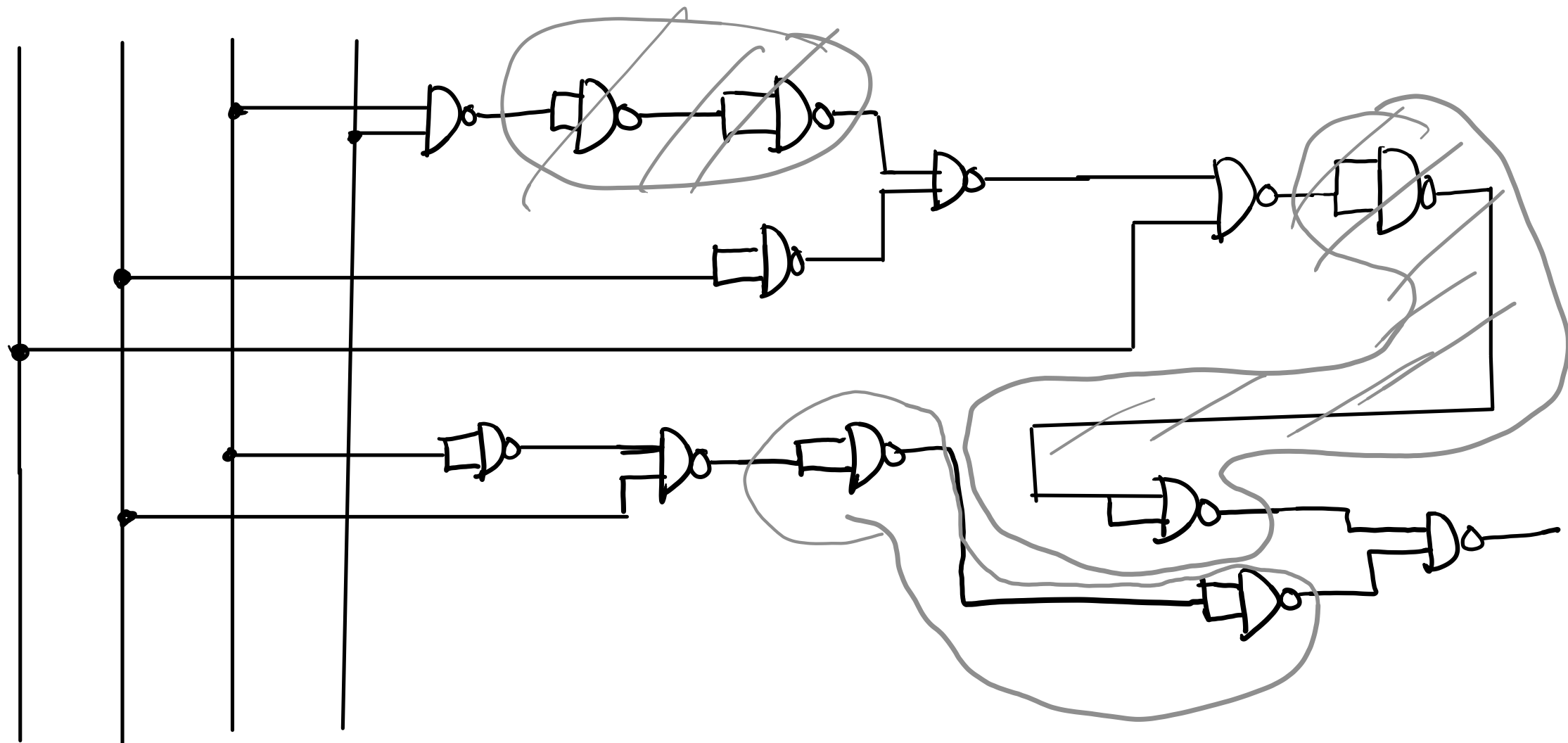

Therefore

A B C D

